

EEL1010 Introduction to Electrical Engineering


Lab Report

Roll Number	B21CH013
Name	Kshitij Aphale
Experiment Number	7
Experiment Title	Thevenin's Theorem in AC Circuits

Objective


To verify the Thevenin's Theorem in AC circuits (on Falstad simulator)

Circuit Diagram

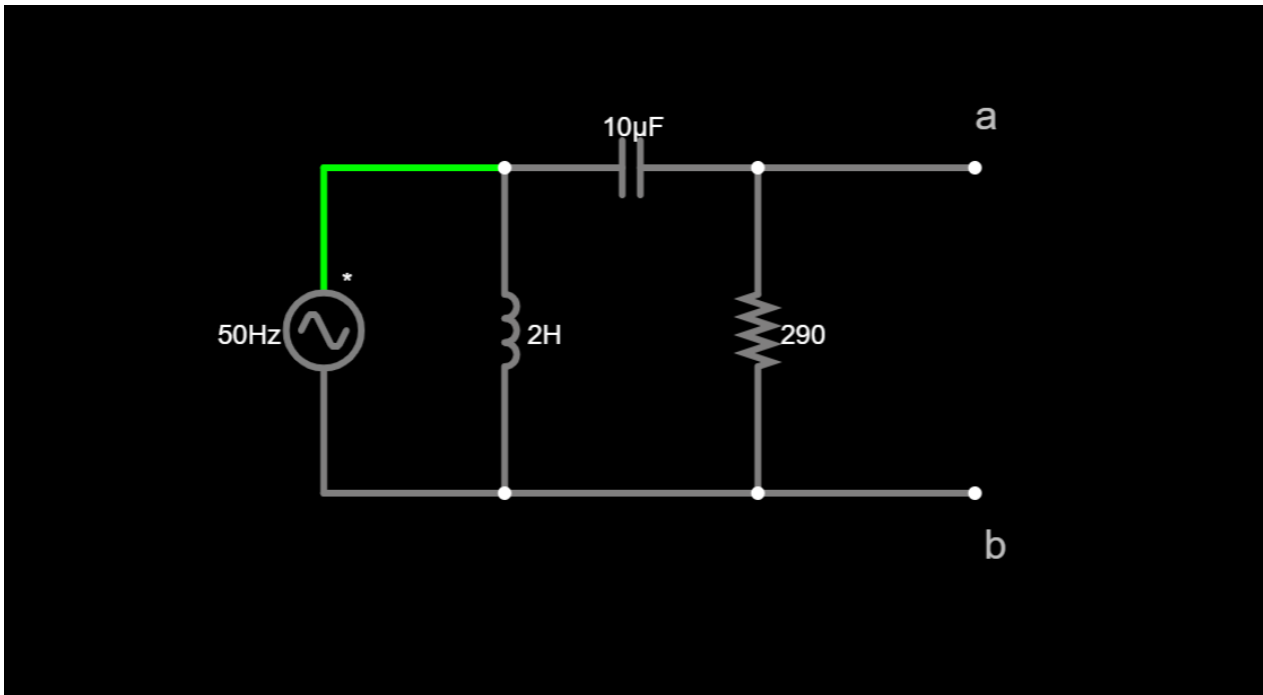


Step 1: Measurement of V_{Th}

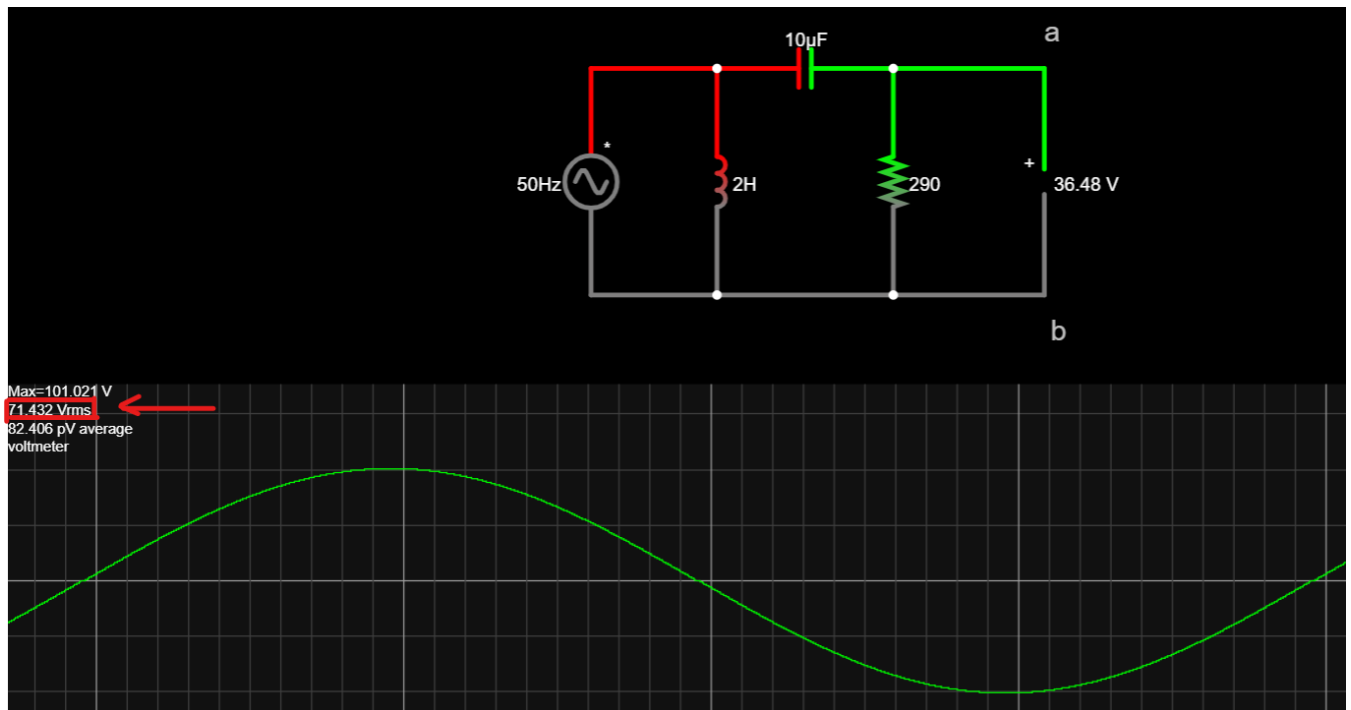From the voltage probe, RMS value of V_{Th} is found to be 71.432V.




Step 2: Measurement of $|Z_{Th}|$

From the voltage probe and ammeter in falstad, RMS value of V_{Test} and I_{Test} is found to be 70.622V and 329.437mA. Hence $|Z_{Th}| = \frac{V_{Test}}{I_{Test}} = \underline{\underline{214.371 \Omega}}$

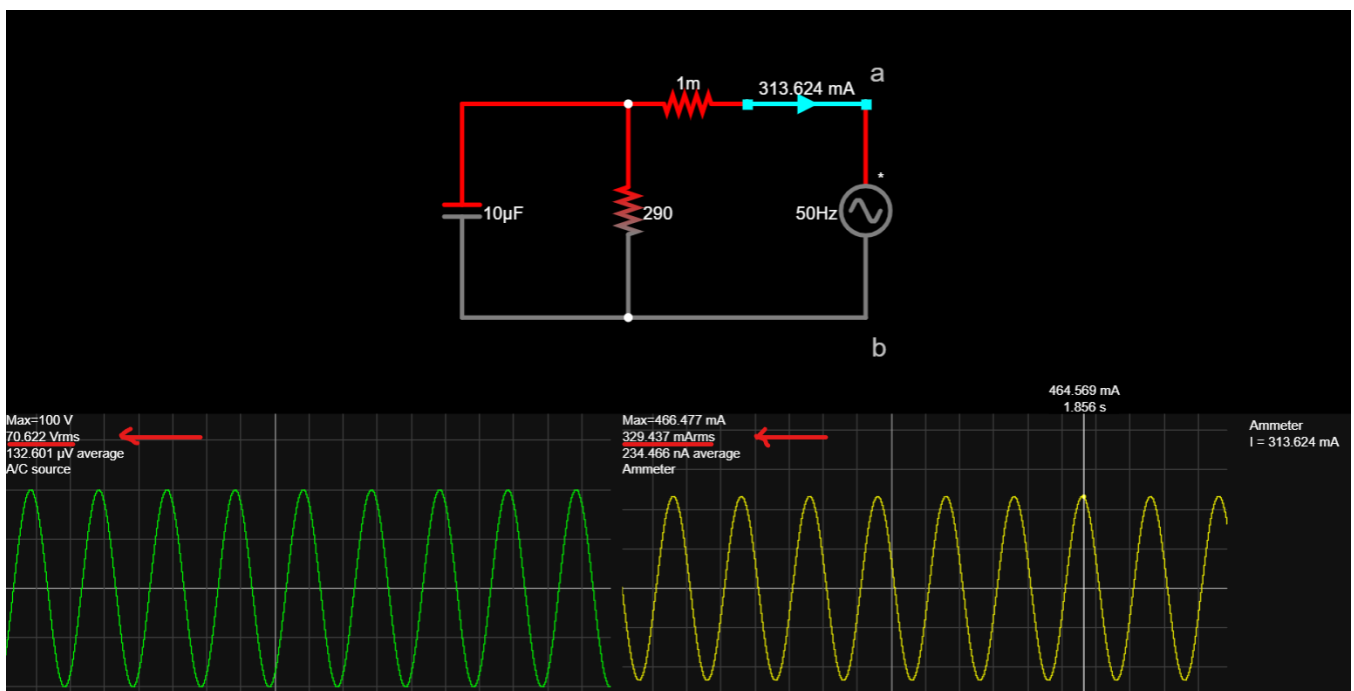

Step 3: Measurement of $\angle Z_{Th}$

From the voltage probe and ammeter in falstad, RMS value of V'_{Test} and I'_{Test} is found to be 70.624V and 207.365mA. Hence $|Z'_{Th}| = \frac{V'_{Test}}{I'_{Test}} = 340.578 \Omega$. After simultaneously solving equations 1 and 2, we get $\angle Z_{Th} = 42.3^\circ$ (Calculations below).

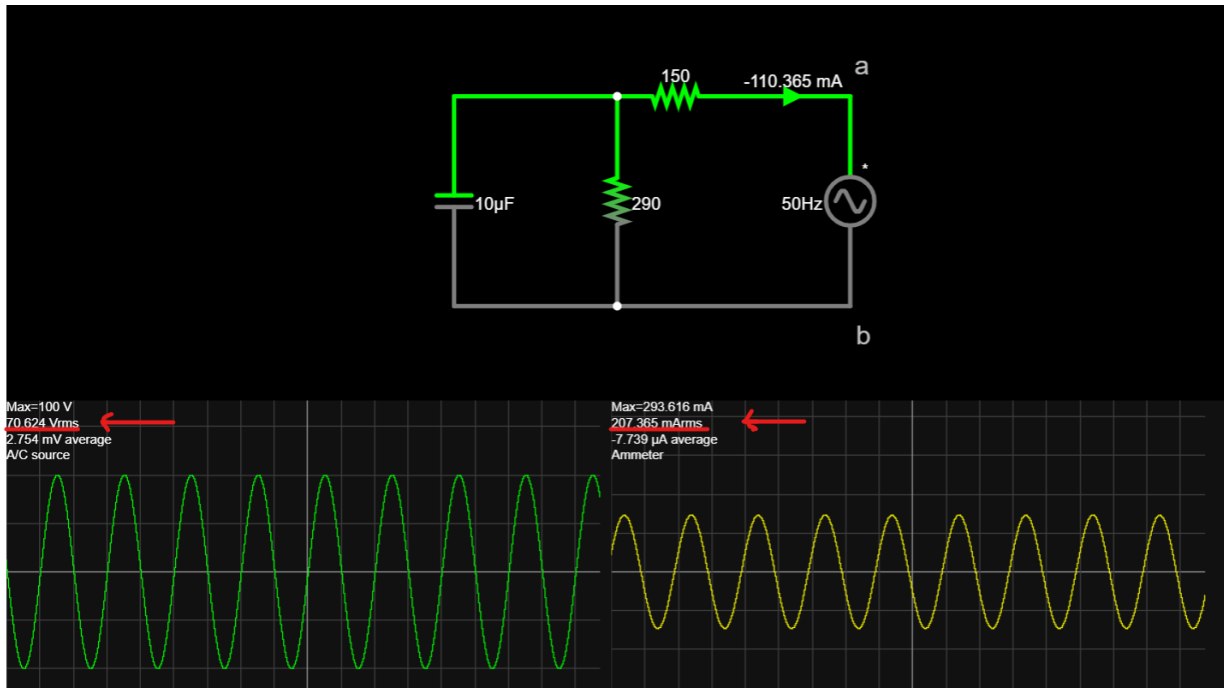

Exp-7

Kshitij Aphale
B21CH013

- ① $\frac{V_{test}}{I_{test}} = \sqrt{(R')^2 + (X')^2} = 214.37$
- ② $\frac{V'_{test}}{I'_{test}} = \sqrt{(R' + 150)^2 + (X')^2} = 340.58$

②² - ①² ⇒

$$(R' + 150)^2 - (R')^2 = 70,040.24$$

$$150(2R' + 150) = 70,040.24$$

$$\therefore R' = \frac{70,040.24}{150} - 150$$

$$\therefore R' = 158.47 \Omega$$

$$\therefore X' = \sqrt{(214.37)^2 - (R')^2}$$

$$X' = 144.37 \Omega$$

$$\therefore \angle Z_{Th} = \tan^{-1}\left(\frac{X'}{R'}\right)$$

$$= \tan^{-1}(0.91)$$

$$\therefore \angle Z_{Th} = 42.3^\circ$$

Step 4: Calculation of Theoretical Values

1. Calculation of $|V_{Th}|$

$$V_{Th} = V_{in} \times \frac{Z_R}{Z_R + Z_C} = V_{in} \times \frac{R}{R + \frac{1}{j\omega C}} = V_{in} \times \frac{j\omega RC}{1 + j\omega RC}$$

Now, $\omega RC = 100\pi \times 290 \times 10 \times 10^{-6} = 0.9$

$$\therefore V_{Th} = V_{in} \left(\frac{0.9j}{1 + 0.9j} \right) = V_{in} \left(\frac{0.9j}{1 + 0.9j} \right) \left(\frac{1 - 0.9j}{1 - 0.9j} \right)$$

$$= \frac{0.9j}{1 + (0.9)^2} + \frac{(0.9)^2}{1 + (0.9)^2} = (0.5)^2 + 0.45$$

$$\therefore |V_{Th}| = \sqrt{(0.5)^2 + (0.45)^2} = 0.672 V_{in}$$

$$V_{Th} = 67.8 V$$

$$= V_{in} \times 0.672$$

$$= \frac{150}{\sqrt{2}} \times 0.672$$

$$|V_{Th}| = 71.276$$

2. Calculation of $|Z_{Th}|$ & $\angle Z_{Th}$

$$Z_{Th} = Z_R \cdot Z_C = \frac{R}{j\omega C} = \frac{R}{R + \frac{1}{j\omega C}} = \frac{R}{1 + j\omega RC}$$

($\omega RC = 0.9$) $\therefore \left(\frac{1}{1 + (0.9)^2} - \frac{0.9j}{1 + (0.9)^2} \right) R$

$$\therefore Z_{Th} = (0.55 - 0.5j) R$$

$$\therefore |Z_{Th}| = \sqrt{(0.55)^2 + (0.5)^2} R$$

$$= 0.743 \times R$$

$$= 0.743 \times 290$$

$$|Z_{Th}| = 215.47 \Omega$$

$$\angle Z_{Th} = 42.27^\circ$$

$|V_{Th}| = 71.276V$

$|Z_{Th}| = 215.47 \Omega$

$\angle Z_{Th} = 42.27^\circ$

Observation Table and Conclusion

Quantity	Theoretical (Calculated)	Experimental (Measured)	Error (%) ((Measured - Theoretical)/Theoretical) × 100
$ V_{Th} $	71.276 V	71.432V	0.21%
$ Z_{Th} $	215.470 Ω	214.371 Ω	-0.51%
$\angle Z_{Th}$	42.27°	42.30°	0.07%

As measured and calculated values are almost same, **Thevenin's theorem is verified**